



For IC1 you can use any common op-amp, such as the tl072, lm358 etc

This circuit will provide amplification to around 11 times up to the limit of the power rails.

[www.dinsync.info](http://www.dinsync.info)

TITLE: diy non inverting amp

Document Number:

REV:

Date: 13/07/2011 08:08:41

Sheet: 1/1